

Quantum Computing Group: Open Project

Title: Building a basic Quantum Adder using Toffoli Gates

By:

Aarav Ratra

Enr: 21122002

Batch: B.Tech Engineering Physics 2021-25

```
In [3]: #Importing basic libraries:

from qiskit import *
from qiskit.tools.visualization import *
import numpy as np
from qiskit.circuit.library import *
```


Step 1: Designing a single full adder circuit

The relations are given as follows:

$S(i) = a(i) \oplus b(i) \oplus C(i-1)$

$C(i) = a(i)b(i) \oplus (a(i) \oplus b(i))C(i-1)$

 Since a generalised toffoli gate can encompass all classical boolean gate operations (AND,OR,NOT,XOR) , we can design the circuits using just CX and CCX gates. The full adder circuit is a 4 qubit circuit and has the following inputs:



(Image referred from the problem statement)

Here is the thinking I have used to design the circuit:

- 1. $a(i)b(i)$ is found to be one of the terms of the carry bit $C(i)$ and is XOR-ed with another quantity. Hence, a toffoli gate is used on $C(i)$ (initialised to $|0\rangle$) with $a(i)$ and $b(i)$ as control qubits. Note that whenever we need an AND boolean relationship, using a CCX gate would be the right direction.
- 2. The quantity $a(i) \oplus b(i)$ is central to both the $S(i)$ bit as well as the $C(i)$ bit. Hence our next step would be to use a CX gate to generate $a(i) \oplus b(i)$ by using $b(i)$ as the target qubit.
- 3. Now, we can easily obtain the required state for $C(i)$ by using a Toffoli with the control bits being the $C(i-1)$ bit and the $a(i) \oplus b(i)$ bit.
- 4. Our last step would be to correctly obtain the SUM bit. That can be obtaining using a simple CX with $C(i-1)$ as our control bit.


```
In [14]: #First, we design a single full-adder circuit
single_adder = QuantumCircuit(4)

#Here, I am letting the registers assigned be as follows:
#q0: C(i-1) (initialised from previous circuit)
#q1: a(i) (will stay unchanged)
#q2: b(i) ==> S(i) (will be changed)
#q3: |0> ==> C(i) (C(i) is 0 by default)

#S(i) = a(i)⊗b(i)⊗C(i-1)
#C(i) = a(i)b(i)⊗(a(i)⊗b(i))C(i-1)


#Qubits in order q0,q1,q2,q3 = C(i-1),a(i),b(i),c(i)[0 by default]
single_adder.ccx(1,2,3)
#Now qubits in order C(i-1),a(i),b(i),a(i)b(i)
single_adder.cx(1,2)
#Now qubits in order C(i-1),a(i),a(i)⊗b(i),a(i)b(i)
single_adder.ccx(0,2,3)
#Now qubits in order C(i-1),a(i),a(i)⊗b(i),C(i-1)(a(i)⊗b(i))⊗a(i)b(i) => Now the carry bit C(i) is holding the required value
single_adder.cx(0,2)
#Now qubits in order C(i-1),a(i),a(i)⊗b(i)⊗C(i-1),C(i-1)(a(i)⊗b(i))⊗a(i)b(i) => Now even the sum bit S(i) (initially b(i)) holds the correct val

single_adder.draw('mpl')
```

 

Step 2: Designing a 4-Bit Quantum Adder using these Single Full Adders

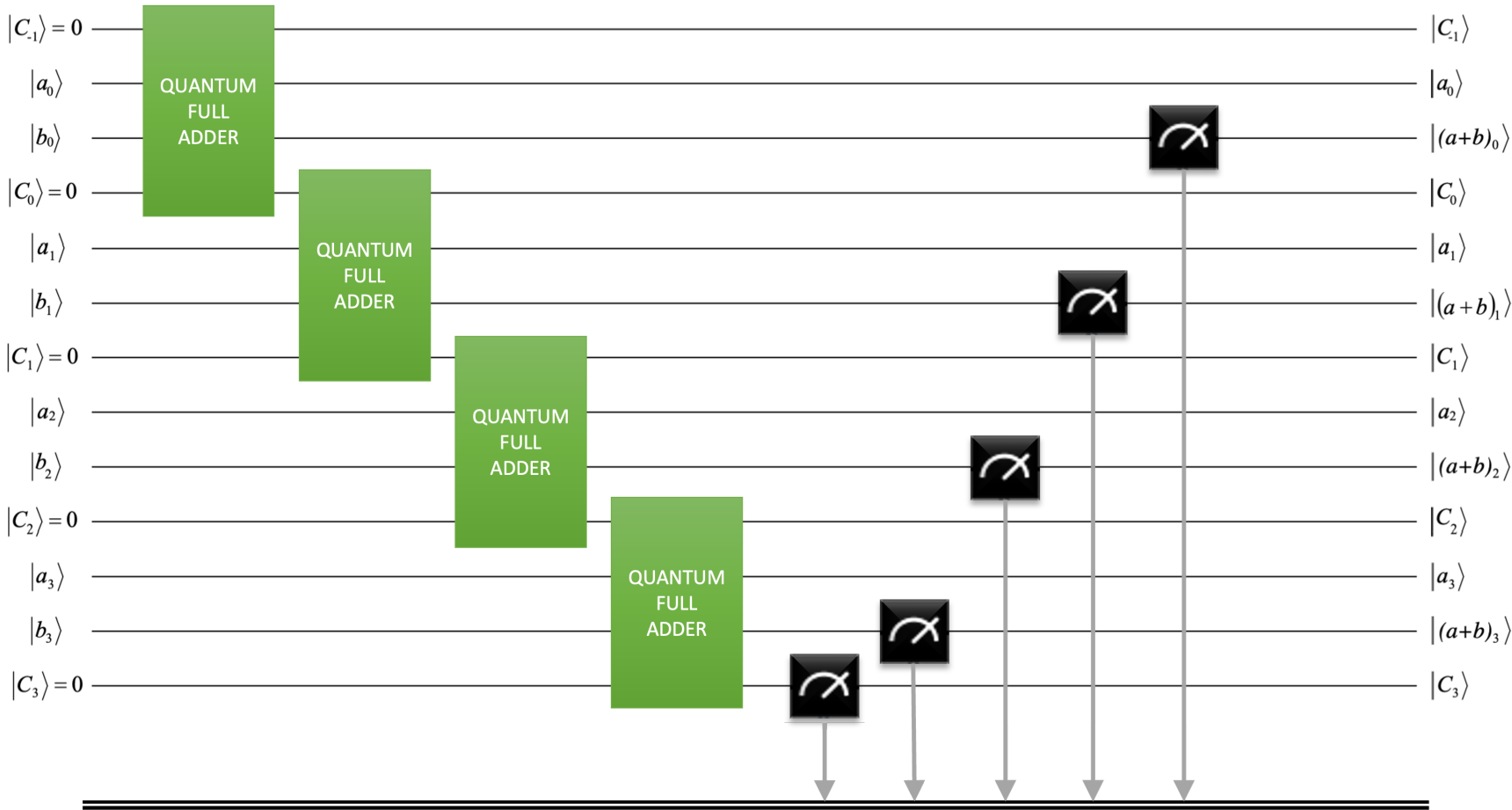Now, we shall design a 4-bit adder using the single full-adder circuit as a module for addition of each bit. All the carry bits (incl $C(-1)$) are initialised to 0 (by default).



I have followed the above skeleton (diagram referred from the problem statement) and used that.

I have defined separate registers for the first bit, 2nd bit and the Carry Bits. For the sake of uniformity/convenience, I have used a separate register containing the C(-1) bit.

Will be defining a separate circuit for the Full Adder, and separate circuits for state initialization.

```
In [16]: #Designing the 4-Bit Quantum Addder


a = QuantumRegister(4,'a')
b = QuantumRegister(4,'b')
C = QuantumRegister(4,'c')
C_1 = QuantumRegister(1,'c_')

cr = ClassicalRegister(5)

adder_4b = QuantumCircuit(a,b,C_1,C,cr)
adder_4b.append(single_adder,[C_1[0],a[0],b[0],C[0]])
adder_4b.append(single_adder,[C[0],a[1],b[1],C[1]])
adder_4b.append(single_adder,[C[1],a[2],b[2],C[2]])
adder_4b.append(single_adder,[C[2],a[3],b[3],C[3]])

adder_4b.measure([C[3],b[3],b[2],b[1],b[0]][::-1],cr)#Measurement order is reversed to obtain our true binary number as Qiskit returns it in rev

adder_4b.draw('mpl')
```

 

Now we shall initialise different states.

I have used H,X and CX gates.

```
In [44]: #STATE 1: A = |0010> , B = |1011>

st1 = QuantumCircuit(a,b)
st1.x(a[1])
st1.x(b[0])
st1.x(b[1])
st1.x(b[3])


qc = QuantumCircuit(a,b,C_1,C,cr)
qc.append(st1,[x for x in a] + [x for x in b])#Initialised state
```

```
qc.append(adder_4b,[x for x in a] + [x for x in b]+[x for x in C_1] + [x for x in C],cr)

qc.draw('mpl')
```

/Users/herobrine127/anaconda3/lib/python3.7/site-packages/qiskit/visualization/matplotlib.py:317: RuntimeWarning: Cregbundle set to False since an instruction needs to refer to individual classical wire
self._get_layer_widths()


Out[44]:

 

```
In [52]: # To obtain solution for STATE 1
simulator=Aer.get_backend('qasm_simulator')
RES=execute(qc,backend=simulator).result()
print(RES.get_counts())
plot_histogram(RES.get_counts())
```

{'01101': 1024}

Out[52]:

 


```
In [57]: #STATE 2: A = |0001> , B = |0011>
st2 = QuantumCircuit(a,b)
st2.x(a[0])
st2.x(b[0])
st2.x(b[1])

qc = QuantumCircuit(a,b,C_1,C,cr)
qc.append(st2,[x for x in a] + [x for x in b])#Initialised state
qc.append(adder_4b,[x for x in a] + [x for x in b]+[x for x in C_1] + [x for x in C],cr)

qc.draw('mpl')
```


Out[57]:

 

In [58]:

```
# To obtain solution for STATE 2
simulator=Aer.get_backend('qasm_simulator')
RES=execute(qc,backend=simulator).result()
print(RES.get_counts())
plot_histogram(RES.get_counts())
```

Out[58]:

 

In [60]:

```
#STATE 3: A = |0010>+|0100> / √2 , B = |1011> + |0001> /√2
st3 = QuantumCircuit(a,b)


st3.h(a[2])
st3.x(a[1])
st3.cx(a[2],a[1])

st3.x(b[0])
st3.h(b[3])
st3.cx(b[3],b[1])

qc = QuantumCircuit(a,b,C_1,C,cr)
qc.append(st3,[x for x in a] + [x for x in b])#Initialised state
qc.append(adder_4b,[x for x in a] + [x for x in b]+[x for x in C_1] + [x for x in C],cr)

qc.draw('mpl')
```

Out[60]:

 


In [61]:

```
# To obtain solution for STATE 3
simulator=Aer.get_backend('qasm_simulator')
RES=execute(qc,backend=simulator).result()
print(RES.get_counts())
plot_histogram(RES.get_counts())

{'01111': 266, '01101': 264, '00011': 243, '00101': 251}
```

Out[61]:

 

In [62]:

```
#STATE 4: A = |0000>+|0111> / √2 , B = |0111> + |1000> /√2
st4= QuantumCircuit(a,b)


st4.h(a[2])
st4.cx(a[2],a[1])
st4.cx(a[1],a[0])

st4.h(b[3])
st4.cx(b[3],b[2])
st4.cx(b[2],b[1])
st4.cx(b[1],b[0])
st4.x(b[3])

qc = QuantumCircuit(a,b,C_1,C,cr)
qc.append(st4,[x for x in a] + [x for x in b])#Initialised state
qc.append(adder_4b,[x for x in a] + [x for x in b]+[x for x in C_1] + [x for x in C],cr)

qc.draw('mpl')
```


Out[62]:

 

```
In [63]: # To obtain solution for STATE 4
simulator=Aer.get_backend('qasm_simulator')
RES=execute(qc,backend=simulator).result()
print(RES.get_counts())
plot_histogram(RES.get_counts())
```

{'01000': 287, '00111': 229, '01111': 272, '01110': 236}

Out[63]:

 

Bonus Task #1: If the qubits of registers A and B are entangled

In the above cases, it was clearly seen that Quantum Full Adders would work if the bits a and b were superpositions, hence can be used for finding all possible addition combinations.

Now, we shall see a case where the registers A and B are such that they are entangled. Will take a few test cases:

- 1. $|a\rangle|b\rangle = (|0000\rangle|0000\rangle + |1111\rangle|1111\rangle)/\sqrt{2}$
- 2. $|a\rangle|b\rangle = (|0101\rangle|0101\rangle + |1010\rangle|1010\rangle)/\sqrt{2}$


```
In [68]: #Entangled state 1: |a>|b> = (|0000>|0000> + |1111>|1111>)/sqrt(2)
st_e1= QuantumCircuit(a,b)

st_e1.h(a[3])
st_e1.cx(a[3],a[2])
st_e1.cx(a[2],a[1])
st_e1.cx(a[1],a[0])
st_e1.cx(a[0],b[3])
st_e1.cx(b[3],b[2])
st_e1.cx(b[2],b[1])
st_e1.cx(b[1],b[0])
#This is eqvt to the 8-Qubit GHZ state

qc = QuantumCircuit(a,b,c_1,C,cr)
qc.append(st_e1,[x for x in a] + [x for x in b])#Initialised state
qc.append(adder_4b,[x for x in a] + [x for x in b]+[x for x in c_1] + [x for x in C],cr)

qc.draw('mpl')
```

Out[68]:

 


In [69]:

```
# To obtain solution for Entangled STATE 1
simulator=Aer.get_backend('qasm_simulator')
RES=execute(qc,backend=simulator).result()
print(RES.get_counts())
plot_histogram(RES.get_counts())
```

{'00000': 528, '11110': 496}

Out[69]:

 

In [76]:


```
#Entangled state 2: |a>|b> = (|0101>|0101> + |1010>|1010>)/√2
st_e2= QuantumCircuit(a,b)

st_e2.h(a[3])
st_e2.cx(a[3],a[2])
st_e2.cx(a[2],a[1])
st_e2.cx(a[1],a[0])
st_e2.cx(a[0],b[3])
st_e2.cx(b[3],b[2])
st_e2.cx(b[2],b[1])
st_e2.cx(b[1],b[0])
st_e2.x(a[2])
st_e2.x(a[0])
st_e2.x(b[2])
st_e2.x(b[0])
#This is eqvt to the 8-Qubit GHZ state

qc = QuantumCircuit(a,b,C_1,C,cr)
qc.append(st_e2,[x for x in a] + [x for x in b])#Initialised state
qc.append(adder_4b,[x for x in a] + [x for x in b]+[x for x in C_1] + [x for x in C],cr)


qc.draw('mpl')
```

Out[76]:

 

```
In [77]: # To obtain solution for Entangled STATE 2
simulator=Aer.get_backend('qasm_simulator')
RES=execute(qc,backend=simulator).result()
print(RES.get_counts())
plot_histogram(RES.get_counts())
```

Out[77]:

 

Explanation

We can define our qubit inputs as

$|a\rangle|b\rangle = \sum |a_k\rangle|b_k\rangle = |a_0\rangle|b_0\rangle + |a_1\rangle|b_1\rangle + \dots$

On measurement, we obtain one of the $|a_k\rangle|b_k\rangle$ values, hence when we do multiple shots of the same job we will get all the $|a_k\rangle|b_k\rangle$ values.

In the case of un-entangled registers $|a\rangle$ and $|b\rangle$, we could factor out $|a\rangle$ and $|b\rangle$ and hence instead of expressing as a sum $\sum |a_k\rangle|b_k\rangle$, we can instead refer to it as a product and hence use that to find all the possible summations for diff values of A and B (like solve for all possible combinations of A and B that can occur)

When the qubits are entangled, it becomes impossible to factor them as $|a\rangle$ and $|b\rangle$. And hence we have to always look towards it as a SUM $\sum |a_k\rangle|b_k\rangle$ instead. This would prove useful if we are trying to solve only specific combinations of A and B.

THANK YOU